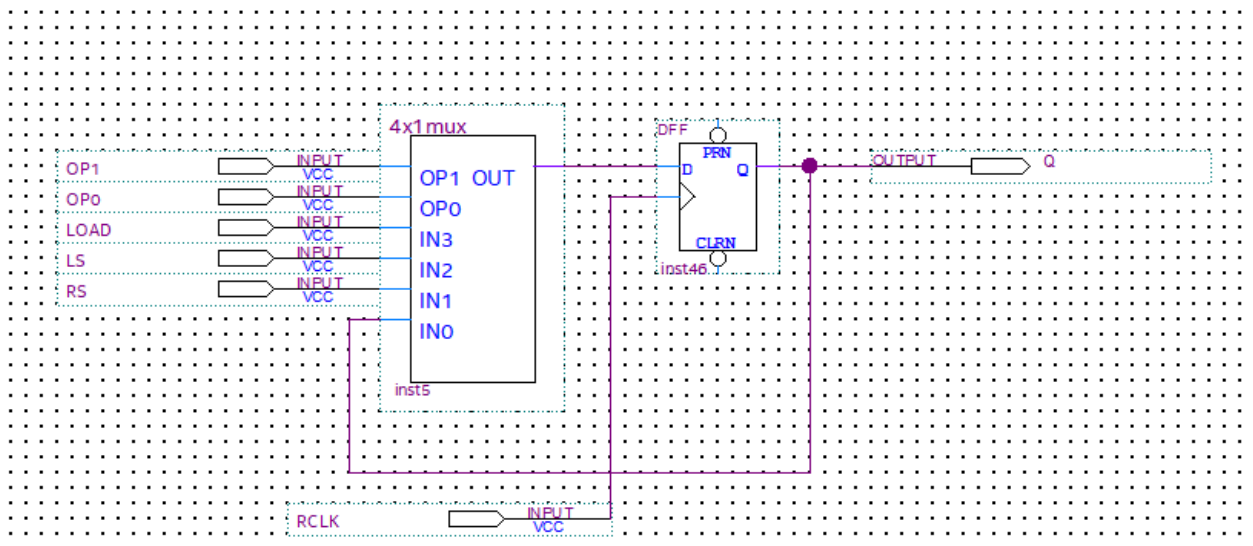



CprE281 Final Project

Calculator: Braydon Clay & Joey Banowetz

Our original idea was to make a calculator that takes in two 8-bit numbers stored in 2's complement, and can perform one of the 5 operations: add, subtract, multiply, divide, and exponentiate. We used the 7 segment decoders to show the numbers in hexadecimal, but showing a negative sign if the user implements a negative number. To add another cool feature to "stand out", we came up with the idea to be able to store a number into an 8 bit register, and to "pull" that number to be reused later (very similar to how modern calculators can do "Ans + x"). We started out first by building a universal 16 bit register, which uses inputs given as OP0 and OP1 to determine the action to be taken. By then linking 16 of these together, we had our 16 bit register.



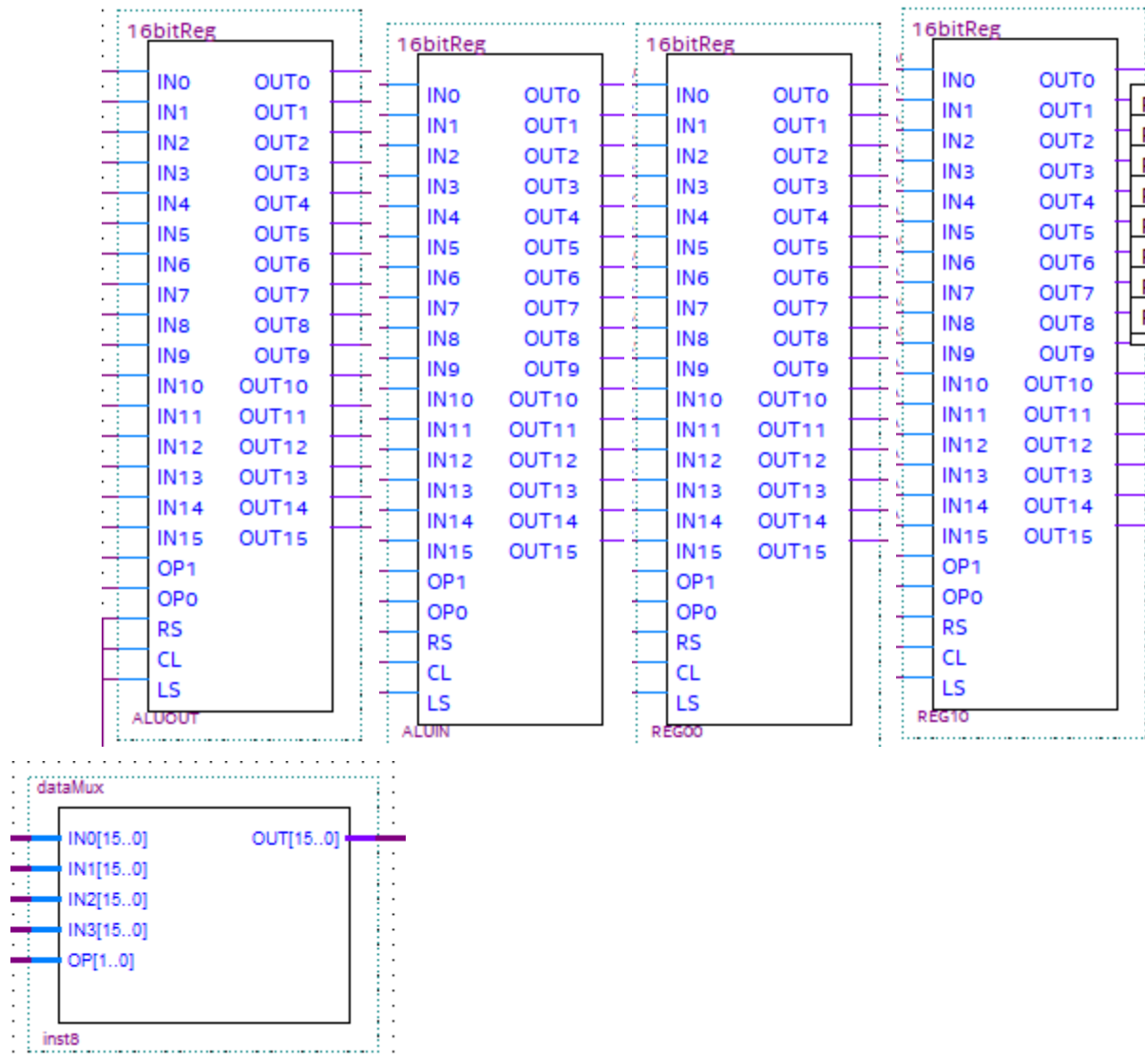We used 4 of these registers total. 2 of these registers were used for storage, and the other 2 were used for the input and output of the entire ALU. We then took all the output of these registers, and fed them into one multiplexer, being our dataMux, with the output from dataMux being the DATA bus line that gave the input throughout the ALU.




```
module dataMux ( input [15:0]IN0, input [15:0]IN1, input [15:0]IN2, input [15:0]IN3, output
[15:0]OUT, input [1:0]OP);
```


```
assign OUT = OP[1] ? (OP[0] ? IN3 : IN2) : (OP[0] ? IN1 : IN0);
endmodule
```

Unfortunately after some testing, we realized that it was not possible to implement multiplication, division, and exponential functions, due to the limitations of the board speed. We realized that for all those operations, it would likely take multiple minutes to complete the operation, and it would not be feasible with this limitation.


For our addition and subtraction, we took the data provided from the dataMux, and ran it into a large operation controller. This is because, if the input OP is 1, it will then use XOR gates to generate the two's complement of the negative number, to then be added. It goes up to 16 bits,

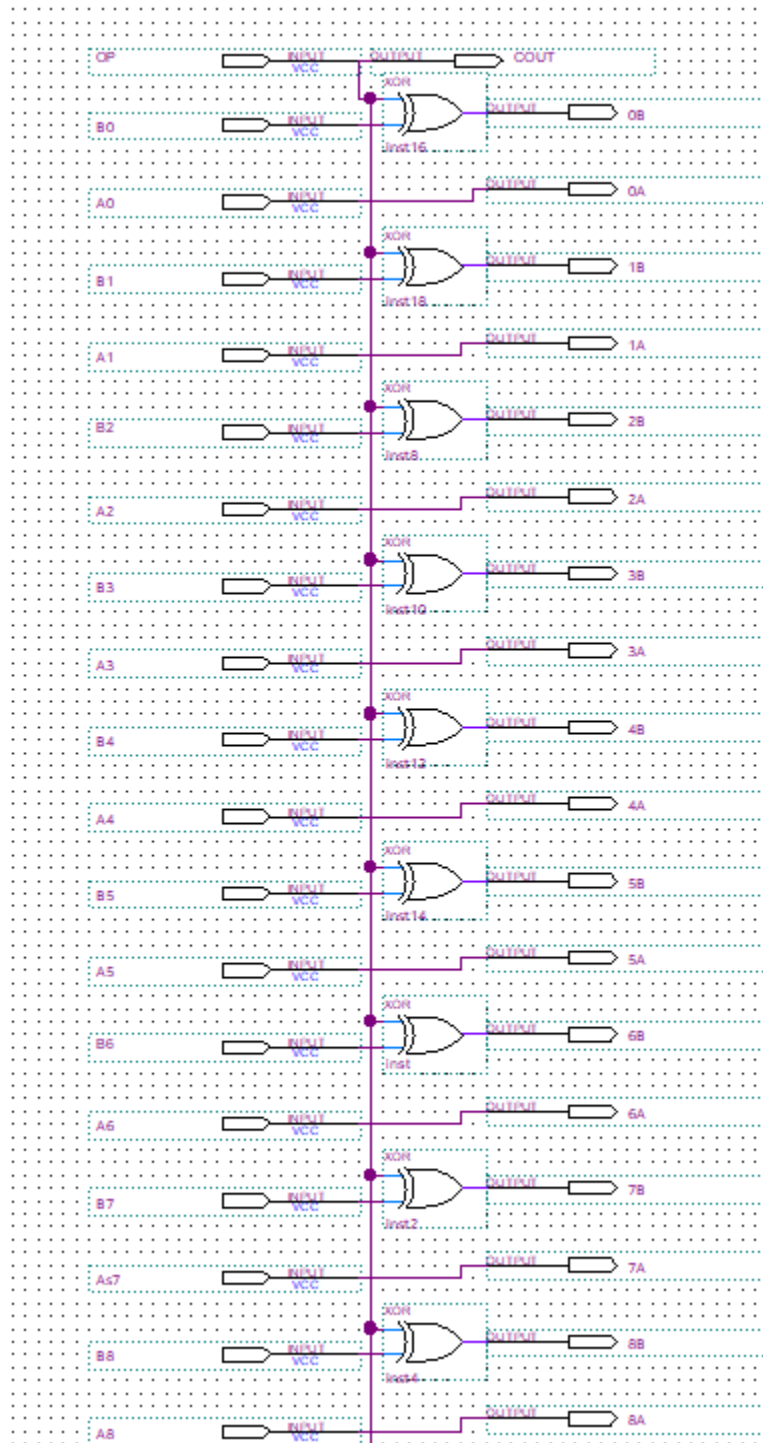as we would also use this for multiplication had we implemented it.




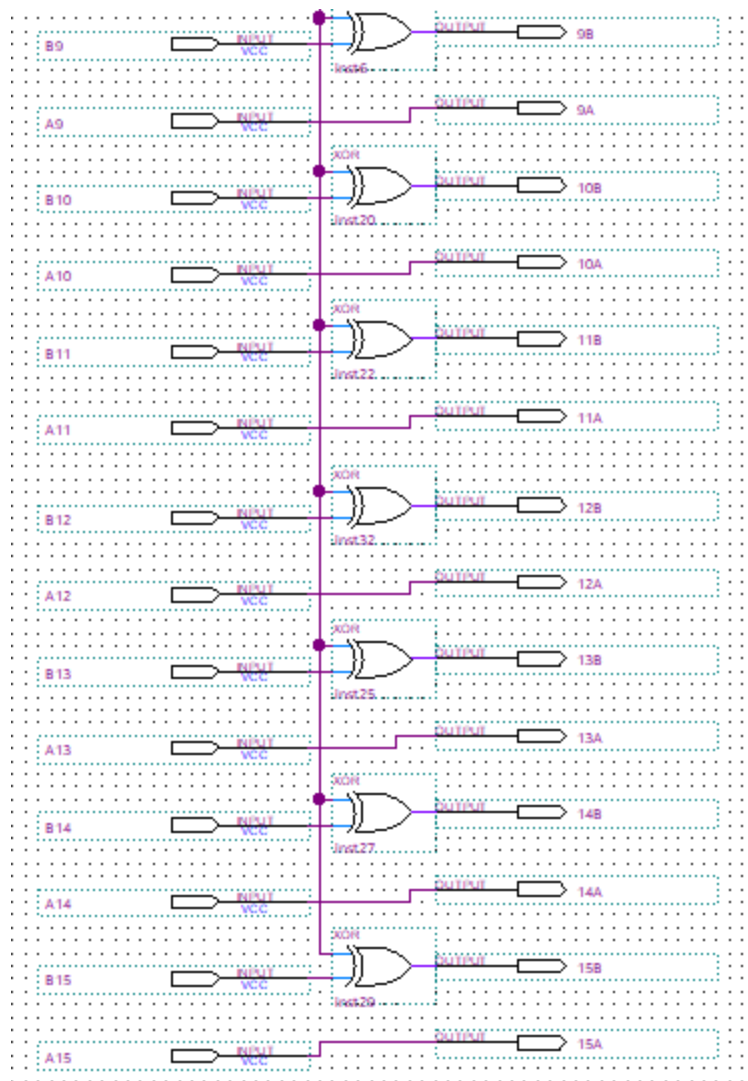

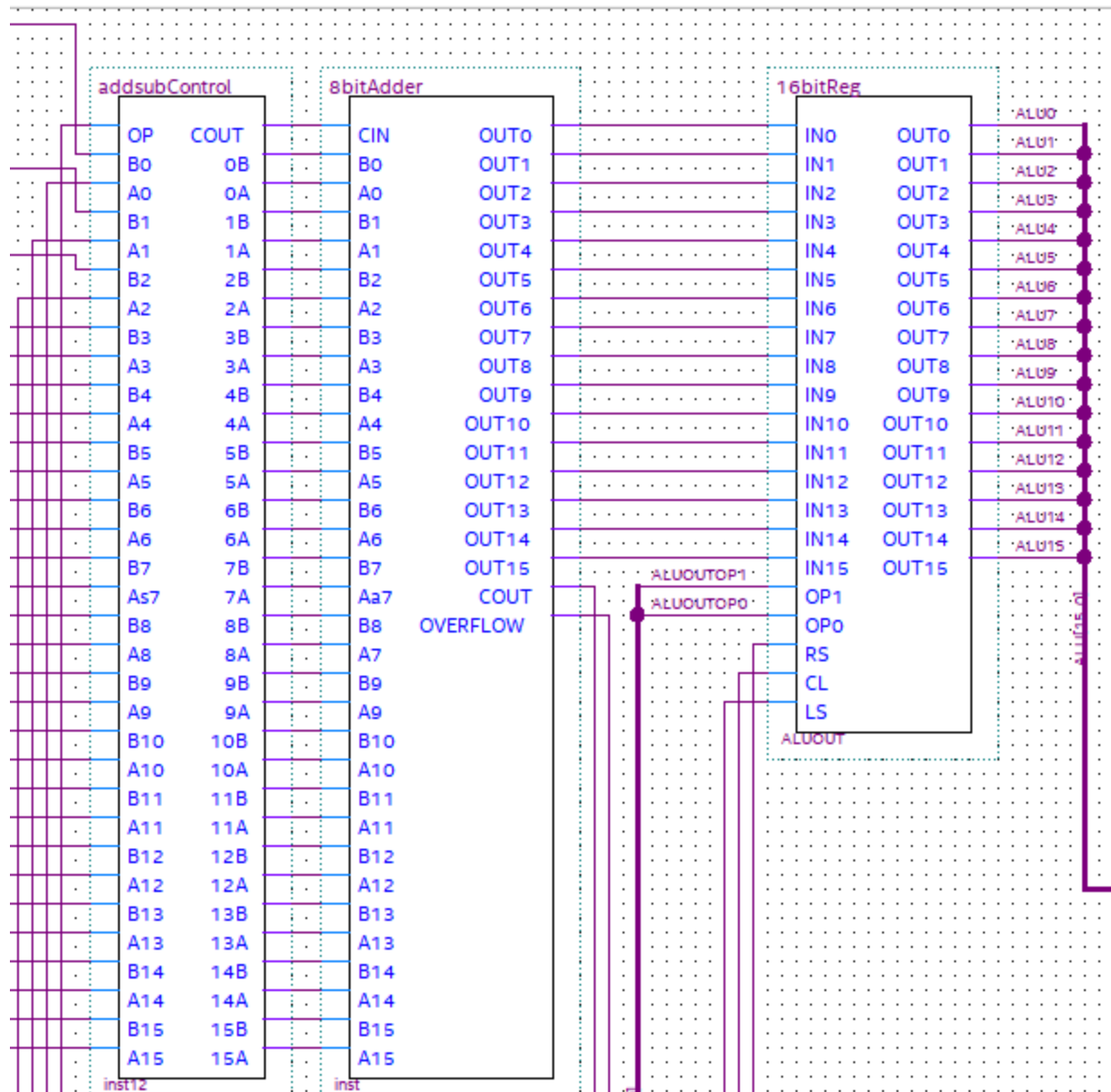
The outputs from the control converter then ran directly into a large adder, which then carried its outputs to “ALUOUT”, with the COUT and OVERFLOW running to the FSM.



General block diagram of the ALU

 


The large 16 bit bit adder

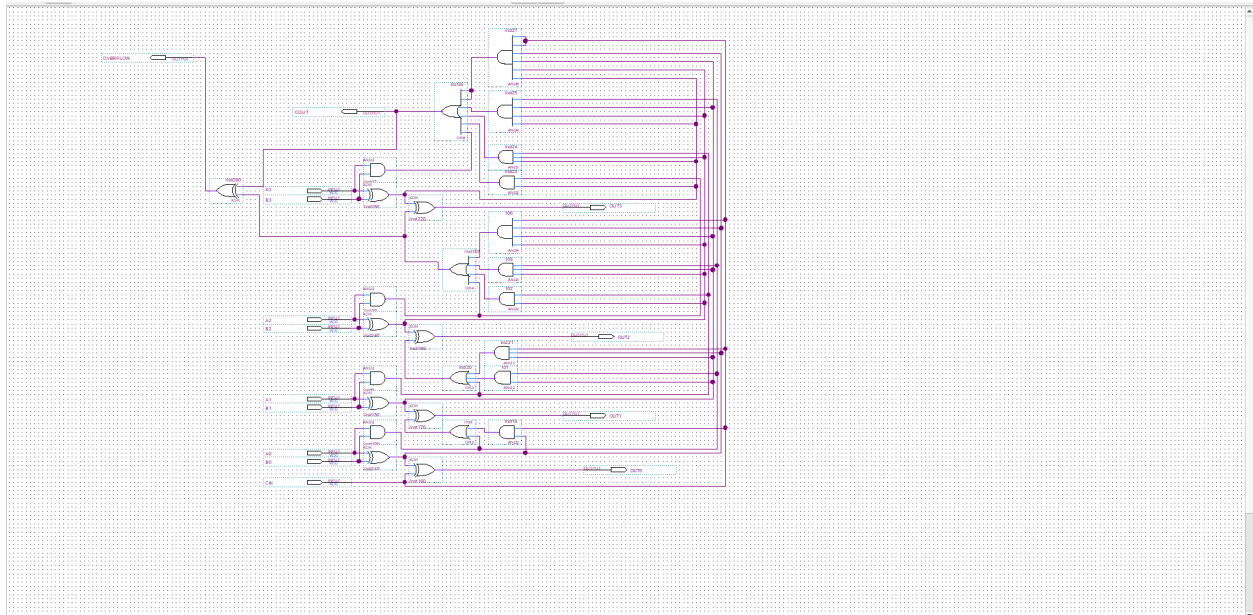



The CLA block diagram used in the adder.

We then had a BUSMUX with the inputs from the operation that had just finished, as well as the output from multiply (which was promptly never used, so the selector is grounded to always be 0). We then ran this then to a 7 segment decoder, which was then used to to show the output with 2 hexadecimal numbers on the board. We also included one segment in a third hexadecimal output for the negative sign, if the number returned is negative.

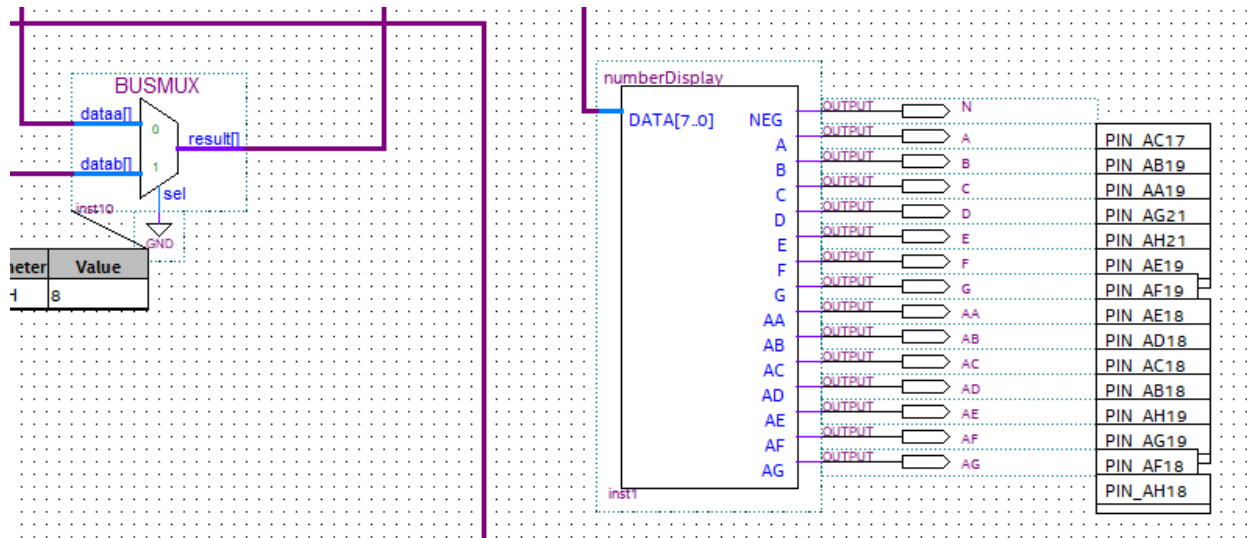


General format in the ALU

 

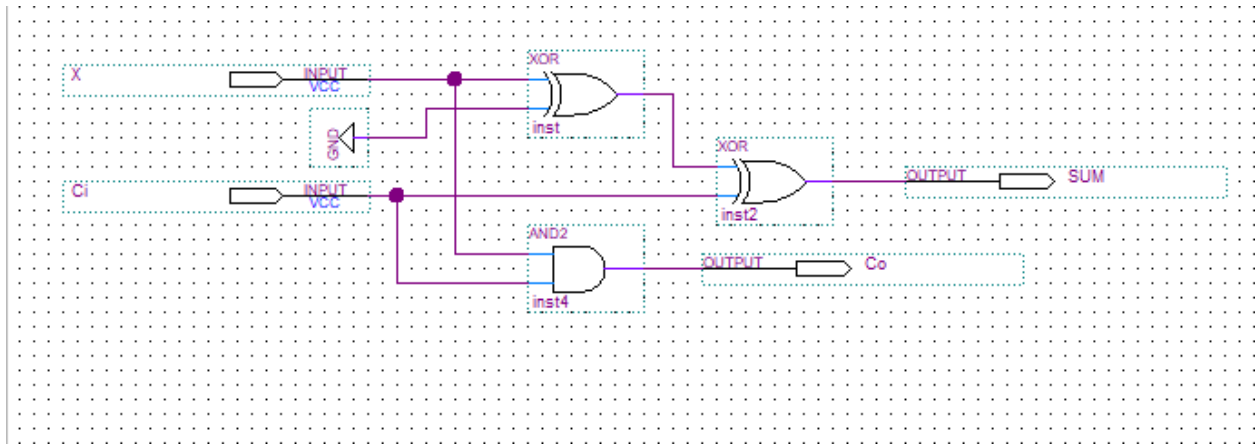

Full adder which was used.

We also included a separate decoder, dependent on which state you were currently in. If you were in the “addition” state, it would show “Add” on the board using the 7 segment. If you were in the “subtraction” state, it would show “Sub” on the board using the 7 segment. As well, we created one for “Mul” if you were in the multiplication state, and “Div” if you were in the division state, though they were never used.

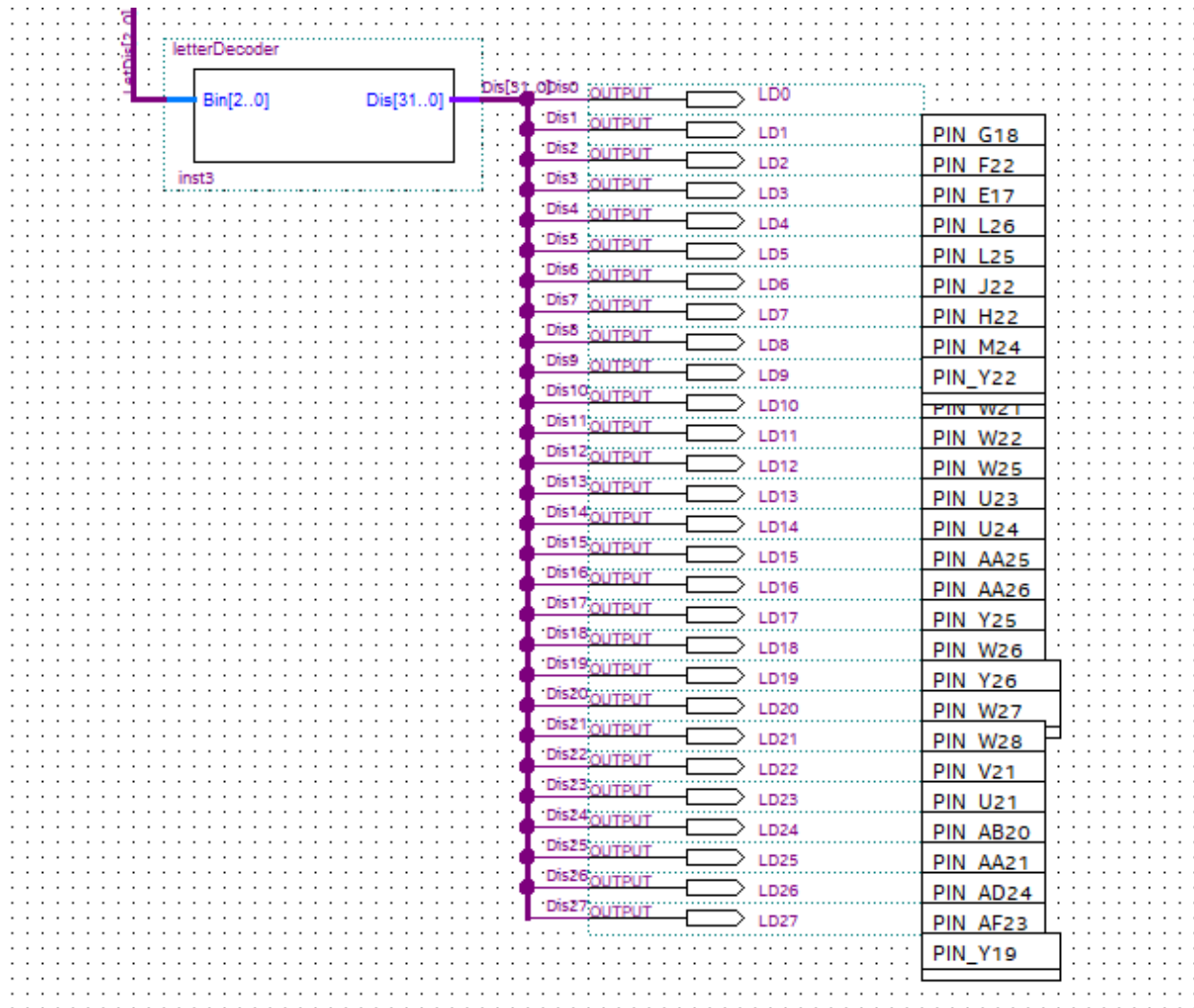

General format in the ALU

```

module letterDecoder(input [2:0]Bin, output reg [31:0]Dis);
always @(Bin)
begin
if(Bin == 3'b000) Dis = 32'b11111111111111111111111111111111;
else if(Bin == 3'b001) Dis = 32'b0010010000100011000110000110;
else if(Bin == 3'b010) Dis = 32'b11111111000100001000010100001;
else if(Bin == 3'b011) Dis = 32'b11111111001001010000010000011;
else if(Bin == 3'b100) Dis = 32'b0001011011101110000011000111;
else if(Bin == 3'b101) Dis = 32'b1111111101000011101111100011;
else Dis = 32'b00000000000000000000000000000000;
end
Endmodule

```

There is a partial implementation of Multiply, which is given below.

```

module multiply (Clock,
Resetn,
LA,
LB,
s,
DataA,
DataB,
P,
Done);
input Clock, Resetn, LA, LB, s;
input [7:0] DataA, DataB;
output [15:0] P;
output reg Done;
wire z;
reg [15:0] DataP;
wire [15:0] A, Sum;
reg [1:0] y, Y;
wire [7:0] B;
reg EA, EB, EP, Psel;
integer k;
parameter S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;
always @(s, y, z)
begin: State_table
    case (y)
        S1: if(s==0)Y=S1;
            else Y = S2;
        S2: if(z==0)Y=S2;
            else Y = S3;
        S3: if(s==1)Y=S3;
            else Y = S1;
        default: Y = 2'bxx;
    endcase
end
always @(posedge Clock, negedge Resetn)
begin: State_flipflops
    if (Resetn == 0) y <= S1;
    else y <= Y;
end

always @(s, y, B[0])
begin: FSM_outputs
    EA = 0; EB = 0; EP = 0; Done = 0; Psel = 0;
    case (y)
        S1: EP=1;
    endcase
end

```

```

        S2: begin
            EA = 1;
            EB = 1;
            Psel = 1;
            if (B[0]) EP = 1;
            else EP = 0;
        end
    S3: Done=1;
endcase
end
//datapath circuit
    shiftrne ShiftB (DataB, LB, EB, 1'b0, Clock, B);
    defparam ShiftB.n = 8;
    shiftrne ShiftA ({8{1'b0}}, DataA}, LA, EA, 1'b0, Clock, A);
    defparam ShiftA.n = 16;
    assign z = (B == 0);
    assign Sum = A + P;
always @(Psel, Sum)
    for (k = 0; k < 16; k = k+1)
        DataP[k] = Psel ? Sum[k] : 1'b0;
    regne RegP (DataP, Clock, Resetn, EP, P); defparam RegP.n = 16;
endmodule

```

Finally, we have the FSM. The FSM started by default, at state A. By then pressing the Key0, you could alternate between user input (state B) and “pull number from register 1” (state C). Once you have found your desired option, you press Key1 to confirm and go to the next part of the process. It will then take you to where you choose your desired operation, being add,sub, and mul, each of these being its own state. In this state, you would also flip switches 7-0 to choose the number you would like as your second number in the operation. By then clicking Key1 again, it will perform the given operation with the two numbers given, and move to the state for output, and it will stay at that output. To use the calculator again, you flip switch 17 off and then back on, to reset the FSM to state A. Below is the code for the FSM.

```

module FSM(
    input [15:0]Data,
    input Overflow,
    input Cout,
    input CLK,
    input Push0,
    input Push1,
    input SW0,
    input SW1,

```

```

input SW2,
input SW3,
input reset,
input done,
output reg enadd,
output reg [1:0]ALUINOP,
output reg ALUINRS,
output reg ALUINLS,
output reg ADDSUB,
output reg [1:0]ALUOUTOP,
output reg ALUOUTRS,
output reg ALUOUTLS,
output reg [1:0]REG0OP,
output reg REG0RS,
output reg REG0LS,
output reg [1:0]REG1OP,
output reg REG1RS,
output reg REG1LS,
output reg [1:0]DATASEL,
output reg [7:0]NumDis,
output reg [2:0]LetDis);

```

```

reg [4:0] x,y;

```

```

parameter [4:0] A = 5'b00000, B = 5'b00001, C = 5'b00010, D = 5'b00011, E = 5'b00100, F =
5'b00101, G = 5'b00110, H = 5'b00111, I = 5'b01000, J = 5'b01001, K = 5'b01010, L = 5'b01011,
M = 5'b01100, N = 5'b01101, O = 5'b01110, P = 5'b01111, Q = 5'b10000, R = 5'b10001, S =
5'b10010, T = 5'b10011, U = 5'b10100, V = 5'b10101, W = 5'b10110, X = 5'b10111, Y =
5'b11000, Z = 5'b11001, AA = 5'b11010, AB = 5'b11011, AC = 5'b11100, AD = 5'b11101, AE =
5'b11110, AF = 5'b11111;

```

```

always @(Push0, Push1, SW0, SW1, SW2, SW3)

```

```

begin: StateTable

```

```

    case (x)

```

```

        A: if(Push0) y = B;
            else if(Push1) y = C;
            else y = A;
        B: if(Push0) y = A;
            else if(Push1) y = C;
            else y = B;
        C: if(Push0) y = D;
            else if(Push1) y = G;//add;
            else y = C;
        D: if(Push0) y = E;

```

```

        else if(Push1) y = I;//sub;
        else y = D;
E: if(Push0) y = C;
    else if(Push1) y = K;//mult;
    else y = E;
G: if(Push0) y = H;
    else if(Push1) y = T;//o;
    else y = G;
H: if(Push0) y = G;
    else if(Push1) y = T;//o;
    else y = H;
I: if(Push0) y = J;
    else if(Push1) y = T;//o;
    else y = I;
J: if(Push0) y = I;
    else if(Push1) y = T;//o;
    else y = J;
K: if(Push0) y = L;
    else if(Push1) y = A;//o;
    else y = K;
L: if(Push0) y = K;
    else if(Push1) y = A;//o;
    else y = L;
T: y = T;
default: y = 5'b00000;
endcase
end
always @(negedge reset, posedge CLK)
begin: State_FlipFlops
    if(reset == 0) x <= A;
    else x <= y;
end

always @(posedge CLK)
begin: Output
    LetDis = 3'b000;ALUINOP = 2'b00; ALUOUTOP = 2'b00; REG0OP = 2'b00; REG1OP =
2'b00;DATASEL = 2'b00;enadd = 1'b1;ADDSUB = 1'b0;
    case (x)
        A: begin
            DATASEL <= 2'b11;
            ALUINOP <= 2'b11;
            NumDis <= Data[7:0];
        end
        B: begin

```

```


        DATASEL <= 2'b01;
        ALUINOP <= 2'b11;
        NumDis <= 8'b00000001;
        LetDis <= 3'b001;
    end
C: begin
    LetDis <= 3'b010;
    NumDis <= 8'b00000000;
    end
D: begin
    LetDis <= 3'b011;
    NumDis <= 8'b00000000;
    end
E: begin
    LetDis <= 3'b100;
    NumDis <= 8'b00000000;
    end
F:   begin
    LetDis <= 3'b101;
    NumDis <= 8'b00000000;
    end
G: begin
    DATASEL <= 2'b11;
    NumDis <= Data[7:0];
    ADDSUB <= 1'b0;
    ALUOUTOP <= 2'b11;
    end
H: begin
    DATASEL <= 2'b01;
    NumDis <= 8'b00000001;
    LetDis <= 3'b001;
    ADDSUB <= 1'b0;
    ALUOUTOP <= 2'b11;
    end
I: begin
    DATASEL <= 2'b11;
    NumDis <= Data[7:0];
    ADDSUB <= 1'b1;
    ALUOUTOP <= 2'b11;
    end
J: begin
    DATASEL <= 2'b01;
    NumDis <= 8'b00000001;
    LetDis <= 3'b001;

```

```

        ADDSUB <= 1'b1;
        ALUOUTOP <= 2'b11;
    end
K: begin
    DATASEL <= 2'b11;
    NumDis <= Data[7:0];
end
L: begin
    DATASEL <= 2'b01;
    NumDis <= Data[7:0];
end
M:
T: begin
    DATASEL <= 2'b00;
    NumDis <= Data[7:0];
    LetDis <= 3'b000;
end
endcase
end
endmodule

```

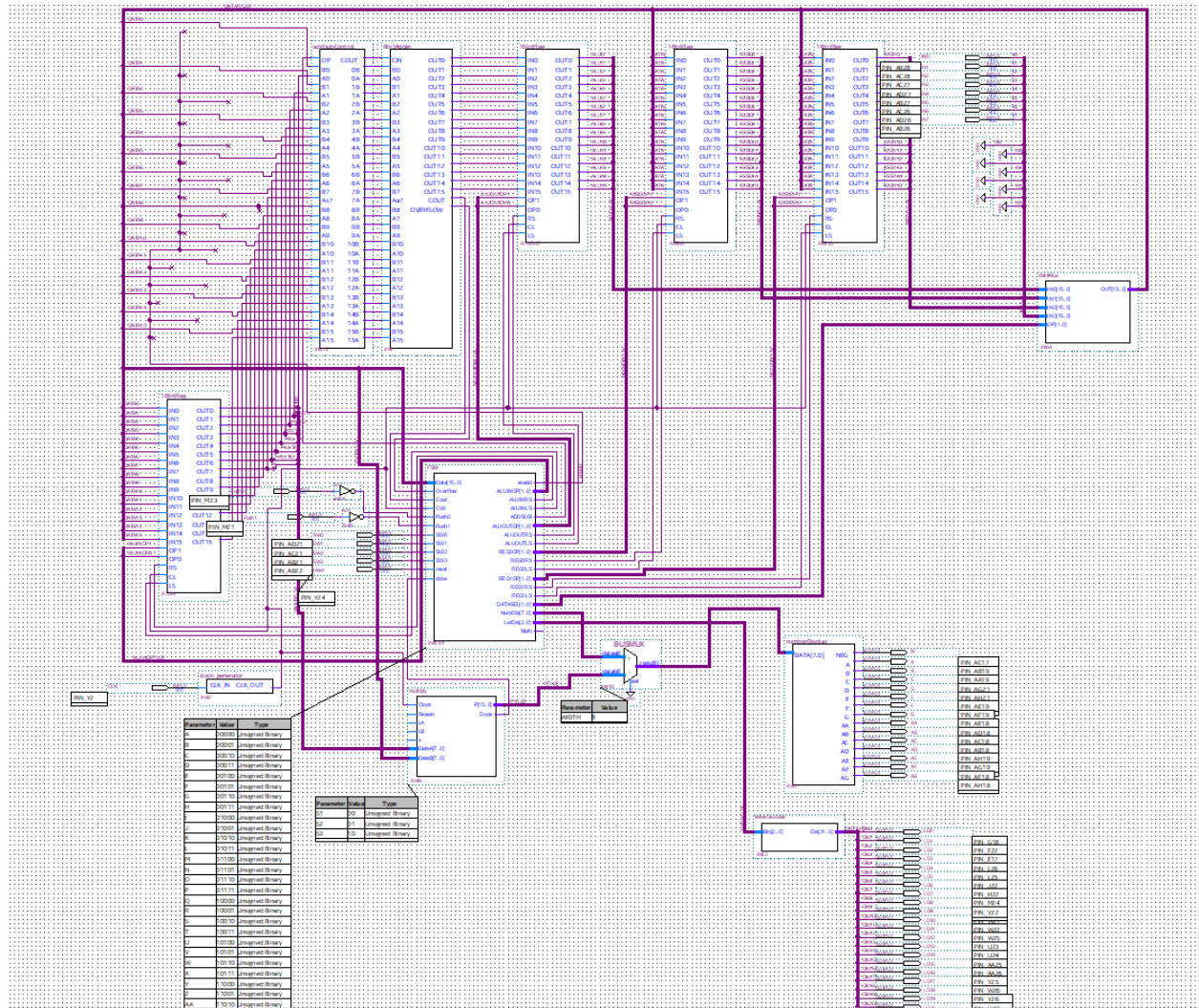This is the diagram of the entire ALU. Below are more zoomed in pictures.



